



American International University- Bangladesh

Final-term Assignment, Fall'2021-22

Subject: Microprocessor and Embedded System

Mark: 30

Submission Deadline: 19/12/2021

Special Instruction: Only the hand-written assignment submitted in PDF is acceptable. Each page of the assignment should contain the 'Name' and 'ID' of the author. Assignment submitted as image/word file without name and ID will get "Zero" and there will be no second chance to submit it again.

Content

1. Design a 1-bit ALU for operations listed in Table-1. [10]
2. Design a 4-bit shifter for the enlisted operation in Table-1. [6]

TABLE 1: FUNCTIONS OF CONTROL VARIABLES

Binary Code	Functions of selection variables					
	A	B	D	F with $C_{in} = 0$	F with $C_{in} = 1$	H
0 0 0	Input Data	Input Data	None	A-1	A	1's to the output Bus
0 0 1	R1	R1	R1	A+B	A+B+1	Shift Left with $I_L=0$
0 1 0	R2	R2	R2	A-B-1	A-B	No Shift
0 1 1	R3	R3	R3	A	A+1	Circulate Left with Carry
1 0 0	R4	R4	R4	\bar{A}	X	0's to the output Bus
1 0 1	R5	R5	R5	A XOR B	X	-
1 1 0	R6	R6	R6	A AND B	X	Circulate-Right with Carry
1 1 1	R7	R7	R7	A OR B	X	Shift Right with $I_R=0$

3. Develop the control memory outputs for the sequence presented in Table-3 using the information listed in Table-1 and 4. In order to complete the memory outputs, use the microinstructions provided below- [14]

TABLE 2: SYMBOLIC MICROPROGRAM FOR CONTROL MEMORY

ROM Address	Microinstruction
0	$X = 1$, if ($q_s = 1$) then (go to 1), if ($q_a = 1$) (then go to 2), if (q_s and $q_a = 0$) then (go to 0)
1	$B_s \leftarrow \bar{B}_s$
2	If ($S = 1$) then (go to 4)
3	$A \leftarrow A + B$, $E \leftarrow C_{out}$ go to 0
4	$A \leftarrow A + \bar{B} + 1$, $E \leftarrow C_{out}$
5	If ($E = 1$) then (go to 0), $E \leftarrow 0$
6	$A \leftarrow \bar{A}$
7	$A \leftarrow A + 1$, $A_s \leftarrow \bar{A}_s$, go to 0

TABLE 3: CONTROL MEMORY BIT SEQUENCE

ROM Address	ROM outputs													
	x	S ₂	S ₁	S ₀	C _{in}	L	y	z	w	Address			Select	
	1	2	3	4	5	6	7	8	9	10	11	12	13	14
0 0 0														
0 0 1														
0 1 0														
0 1 1														
1 0 0														
1 0 1														
1 1 0														
1 1 1														

TABLE 4: MULTIPLEXER INPUT

Rom bits		MUX select function
13	14	
0	0	Load input to CAR
0	1	Increment CAR
1	0	Load input to CAR if $E = 1$, increment CAR if $E = 0$
1	1	Load inputs to CAR if $S = 1$, increment CAR if $S = 0$